
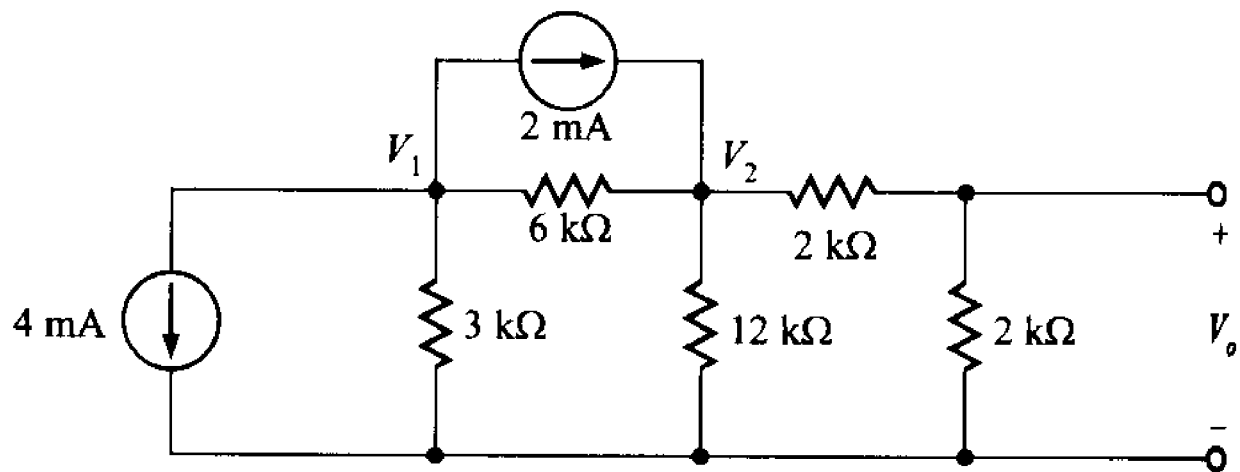


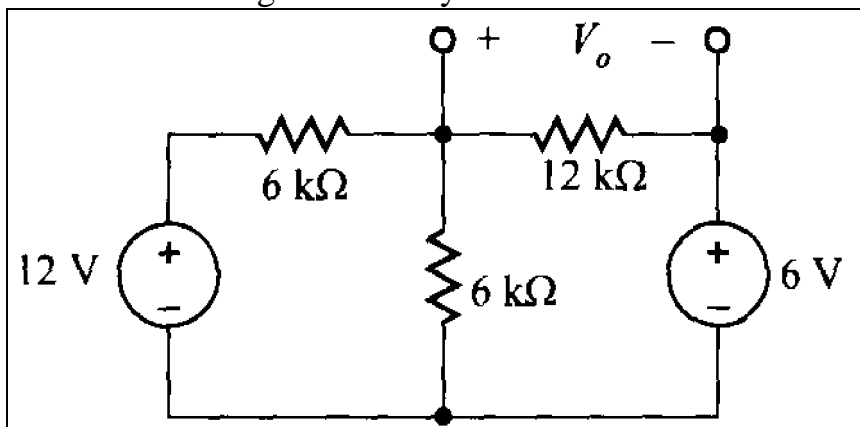
3.3. Use nodal analysis to find both V_1 and V_o in the circuit in Fig. P3.3.




3.6 Find V_o using nodal analysis.




3.14 Find I_o using nodal analysis.

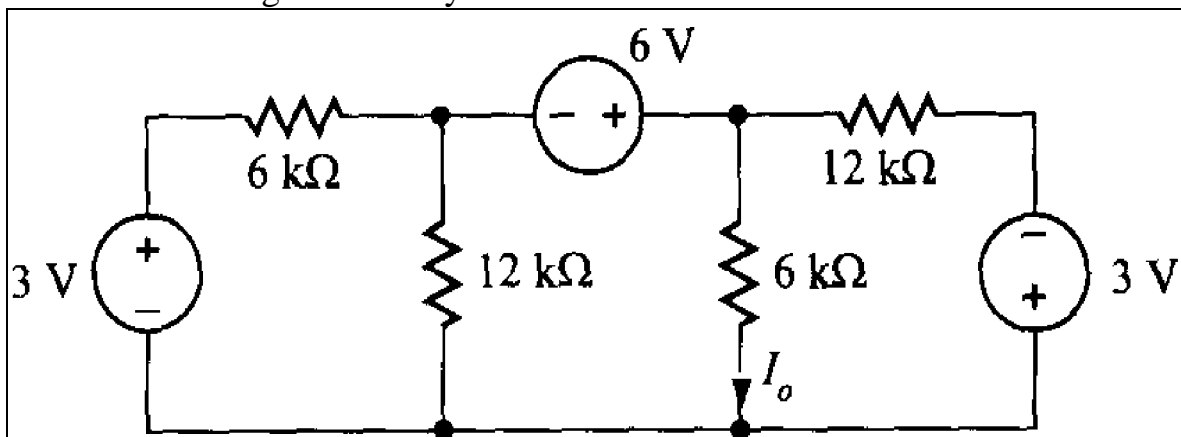

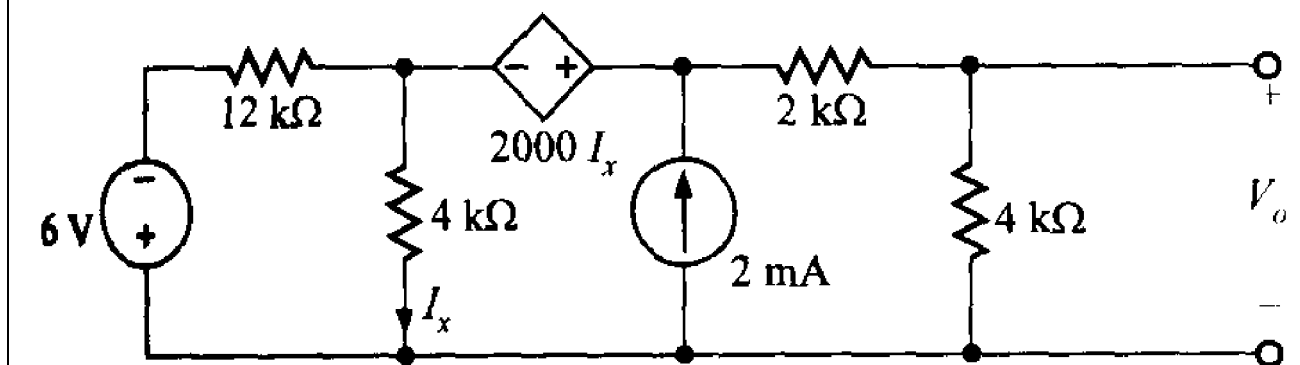
3.24. Find V_o in the circuit in Fig. P3.24. In addition, find all branch currents and check your answers using KCL at every node.



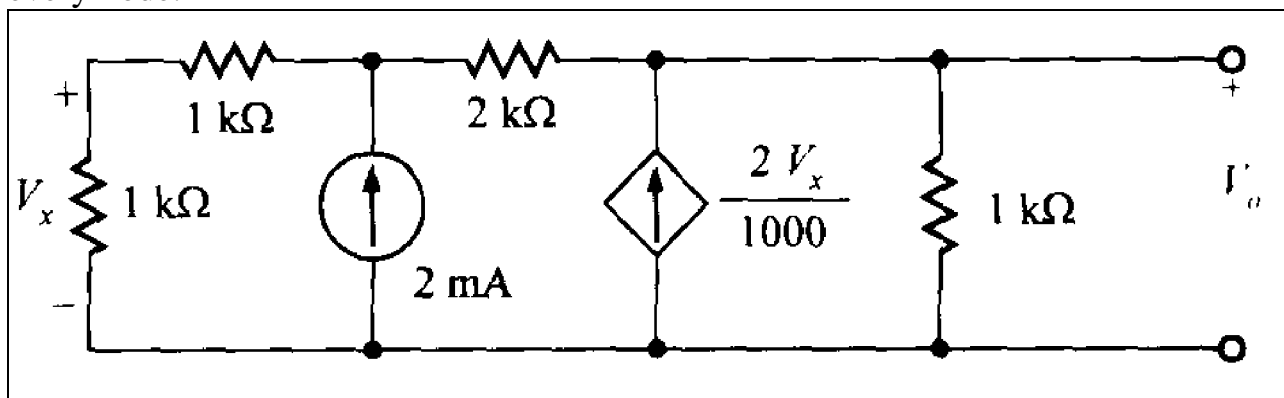
3.26 Find V_o . In addition, find all branch currents and check your answers using KCL at every node.



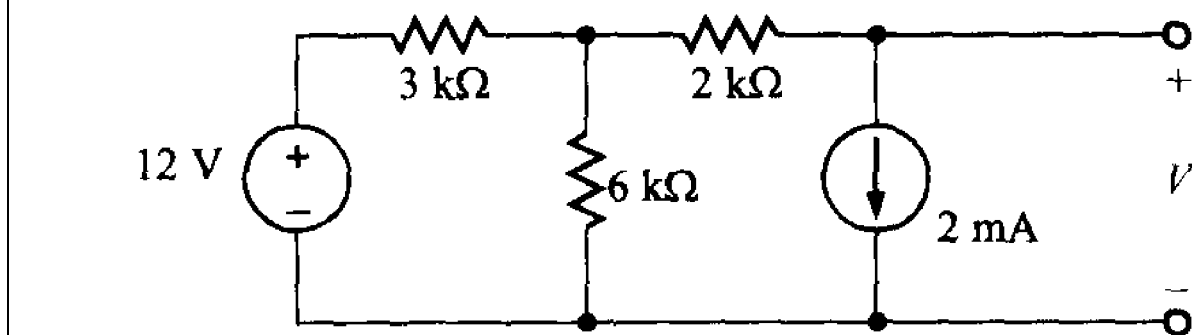
3.31. Use mesh analysis to find V_o in the network in Fig. P3.31.




3.34 Using loop analysis to find I_o .

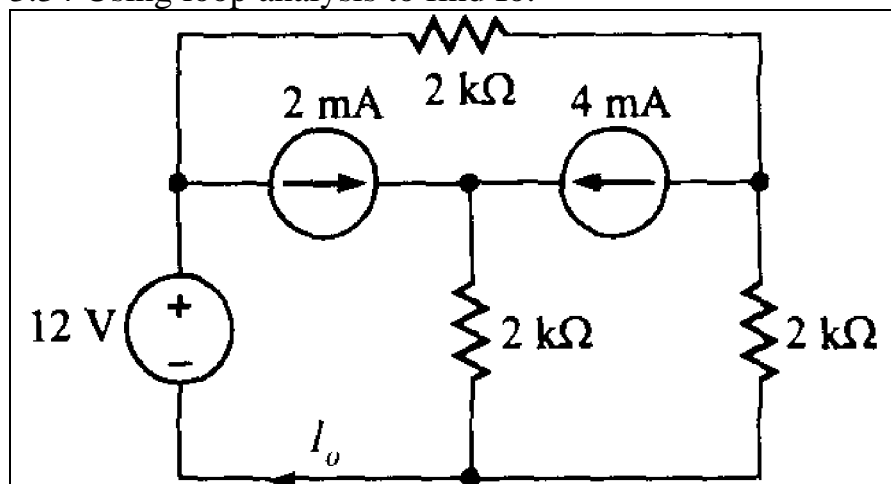

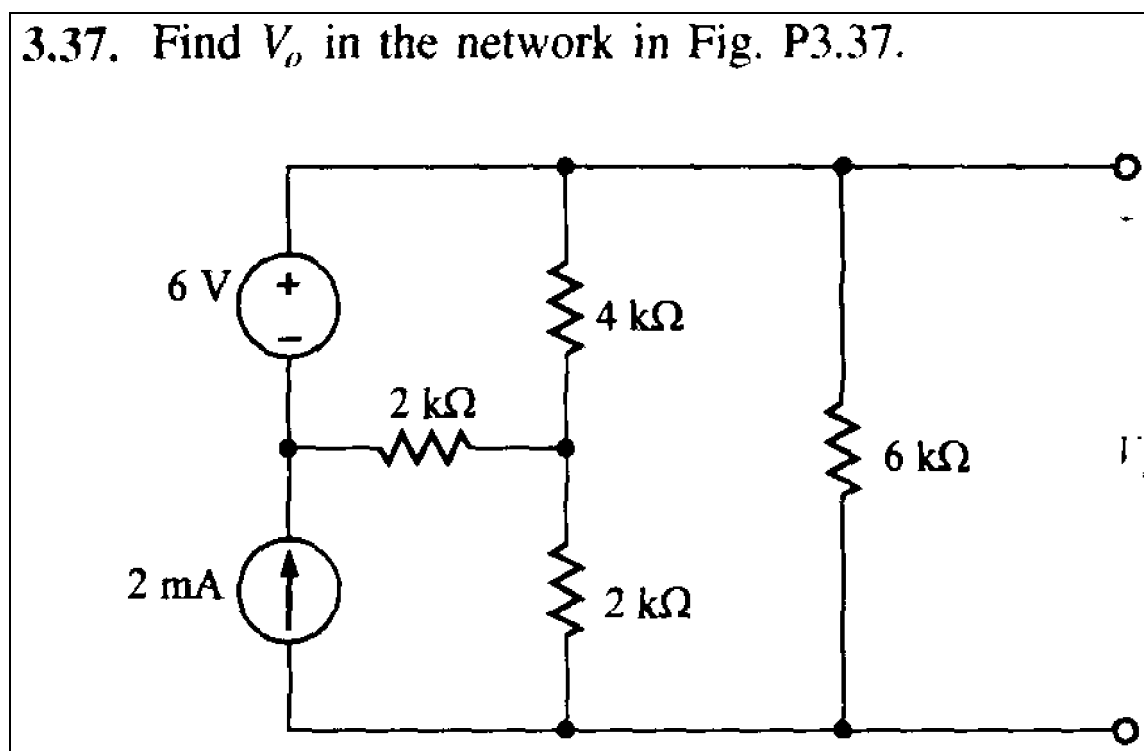3.37. Find V_o in the network in Fig. P3.37.



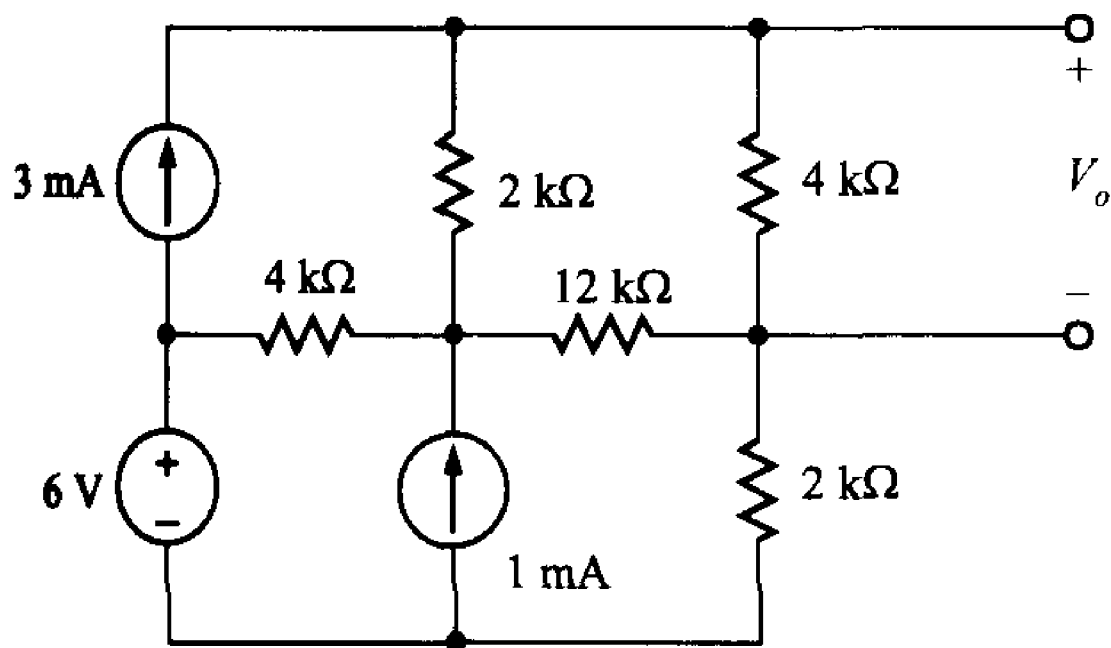3.40. Use loop analysis to find V_o in the network in Fig. P3.40.



3.44. Use loop analysis to find V_o in the circuit in Fig. P3.44.

