
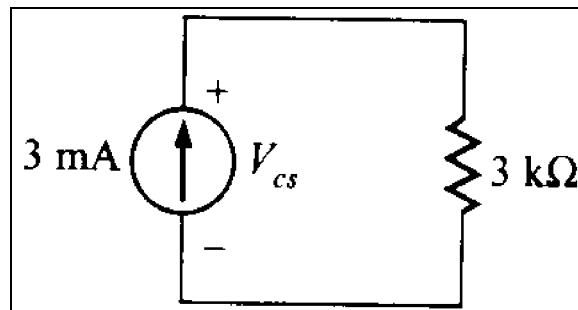


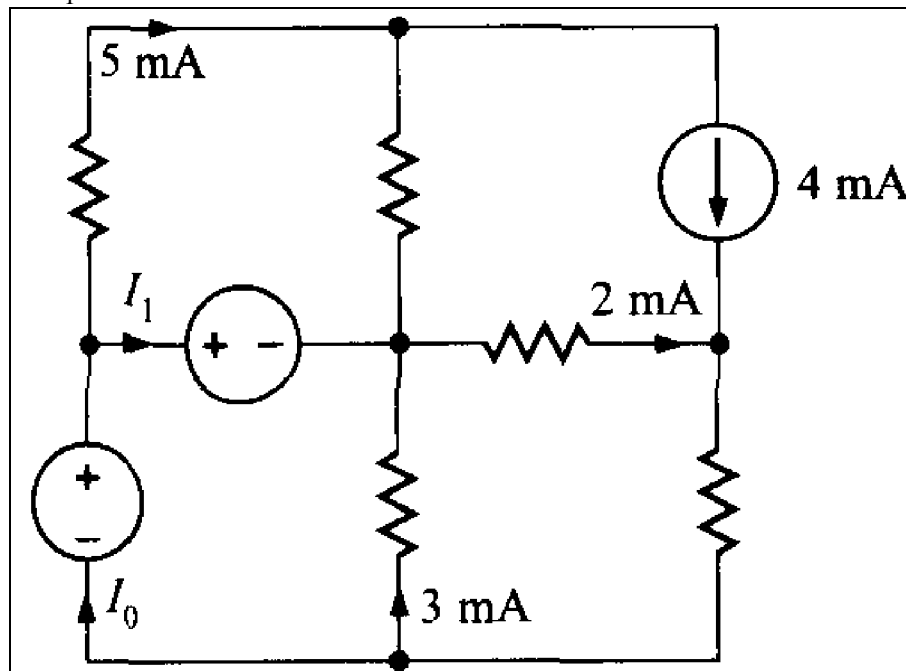
2.5 Find the Voltage across the current source and the power absorbed by the resistor.




2.11 Find I_0 and I_1 .




2.13 Find I_x .

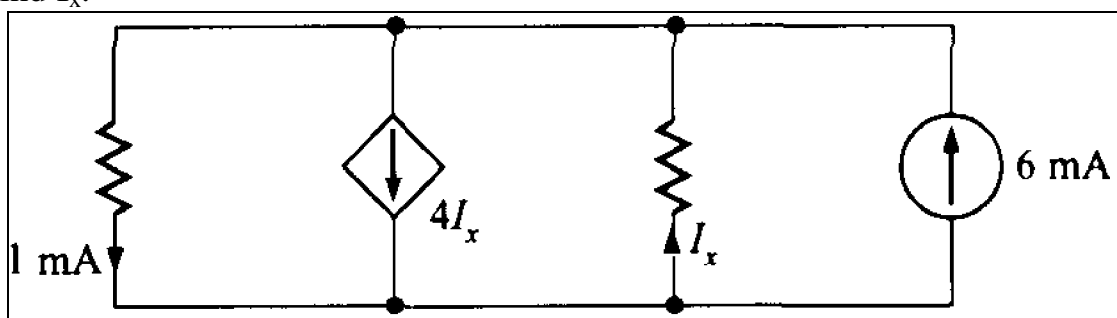


2.16 Find V_{ac} .

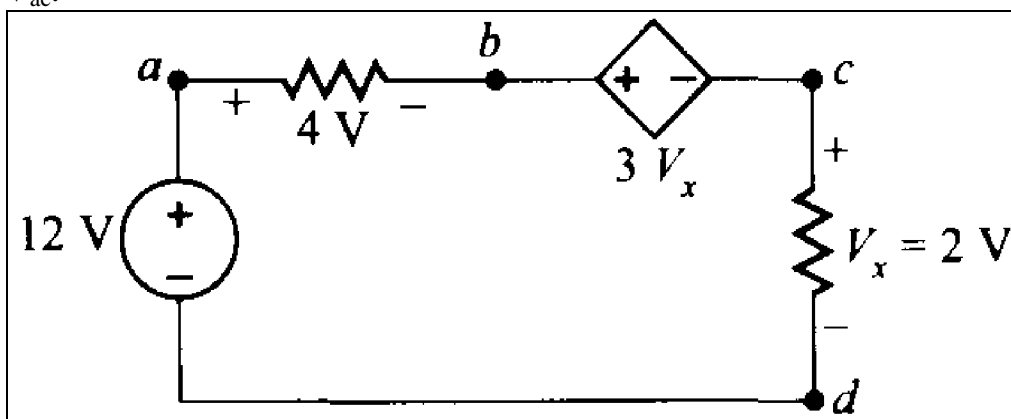


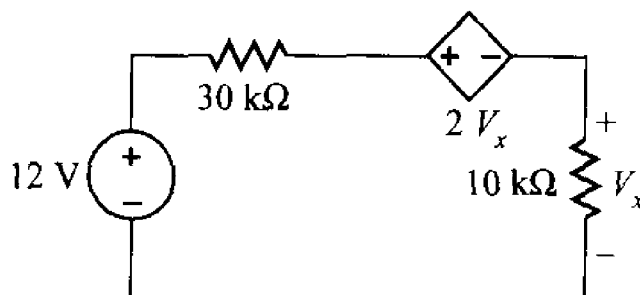2.21. Find the power absorbed by the 30-k Ω resistor in the circuit in Fig. P2.21.




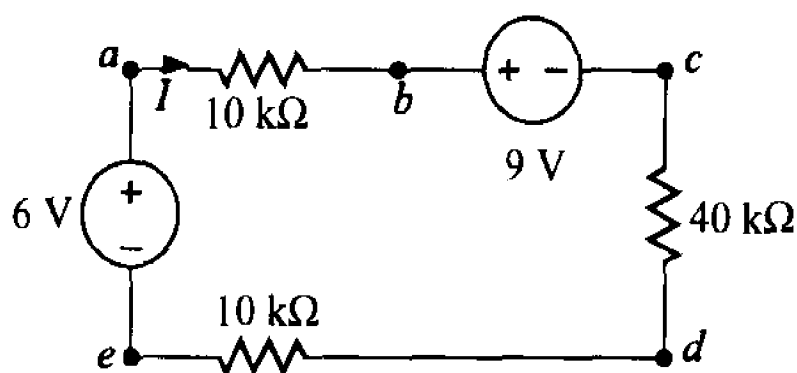2.19. Find both I and V_{bd} in the circuit in Fig. P2.19.




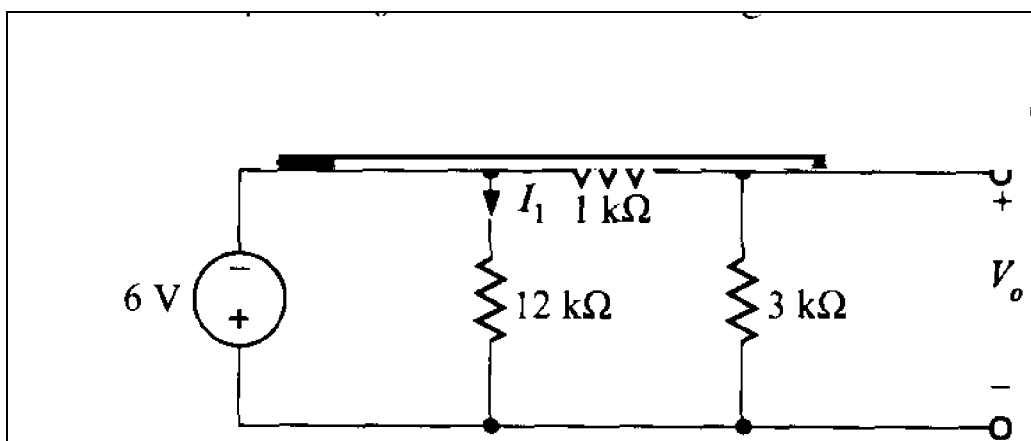

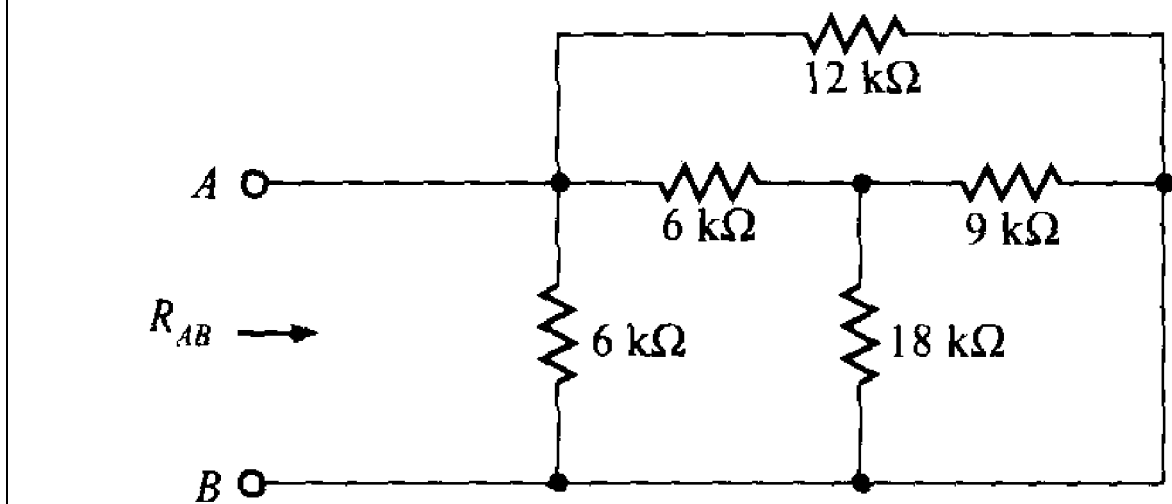
2.30. Find R_{AB} in the network in Fig. P2.30.




2.32 Determine I_o .

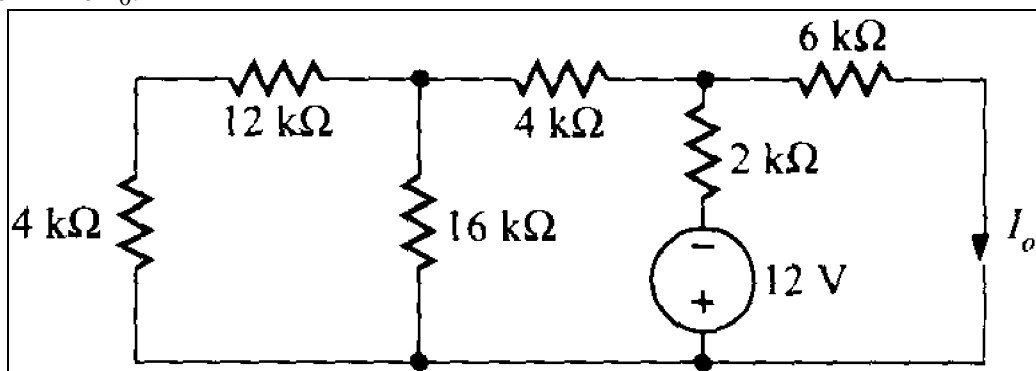


2.36 Find V_o .

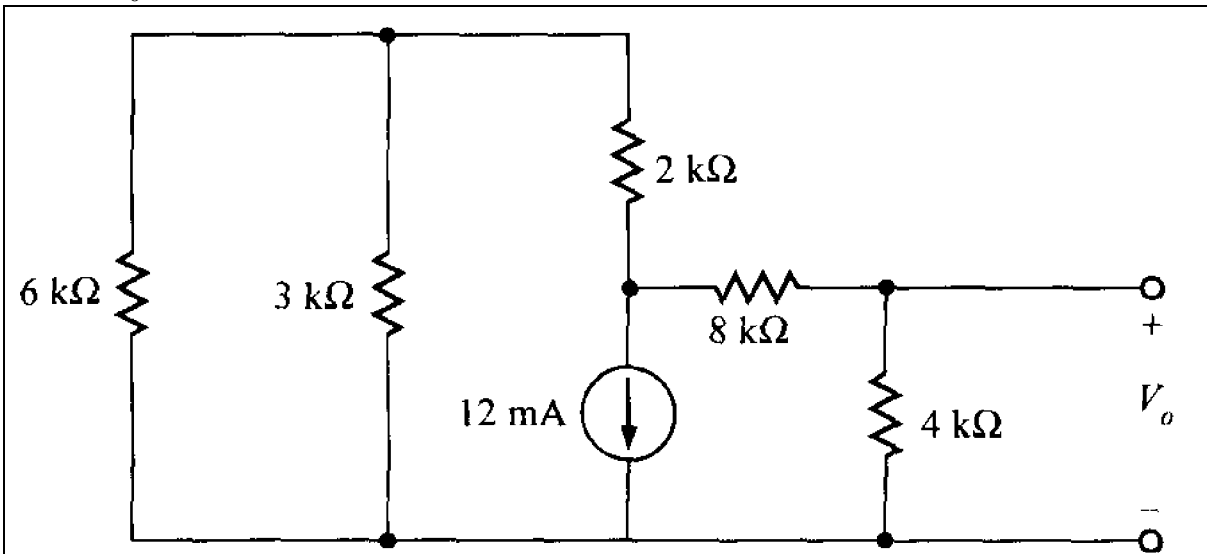


2.41 Find V_o .

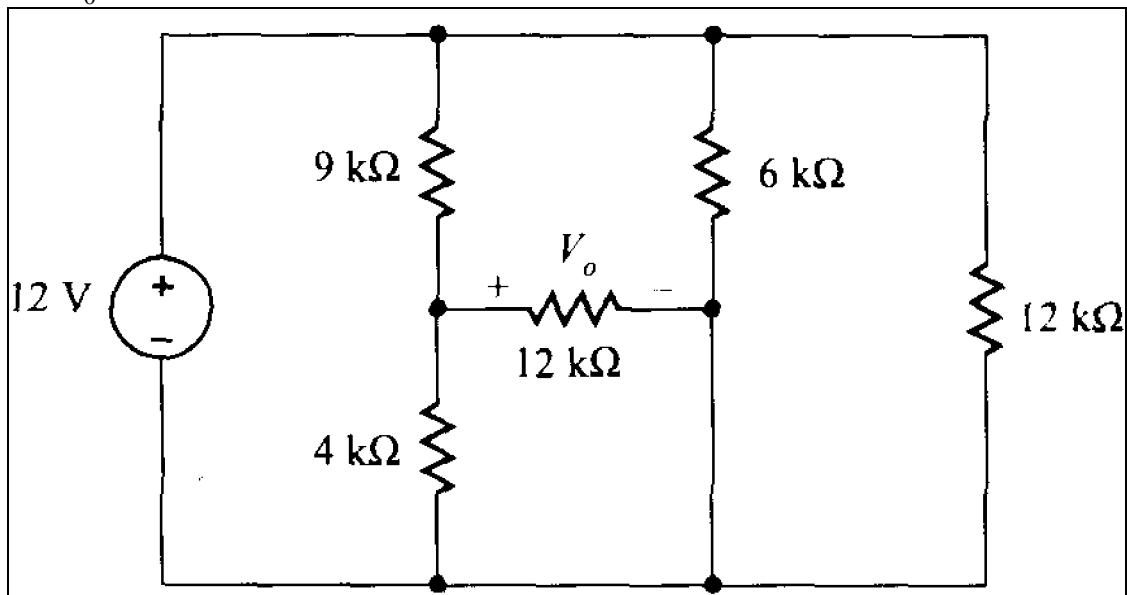

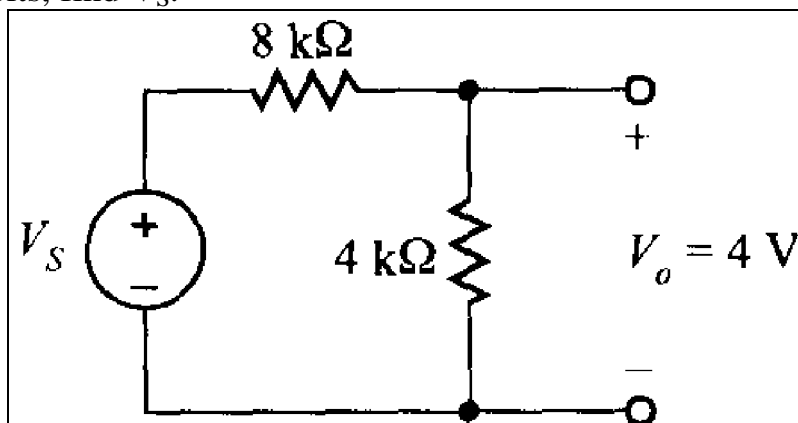
2.47 If $V_o = 4\text{ Volts}$, find V_s .




2.52 If $I_o = 2 \text{ mA}$, find V_S .

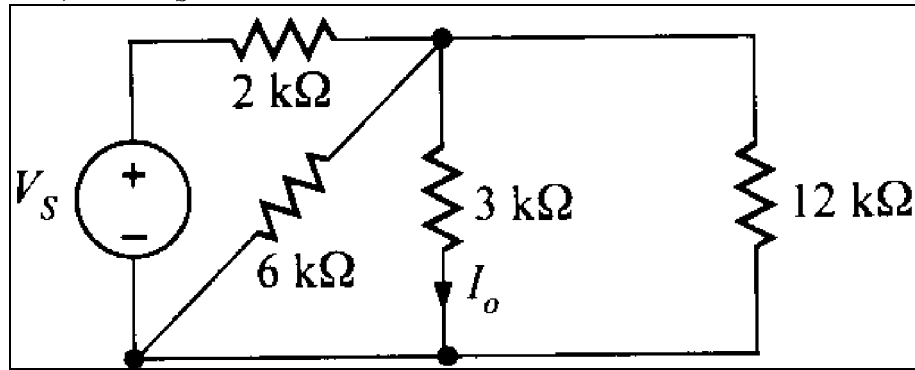

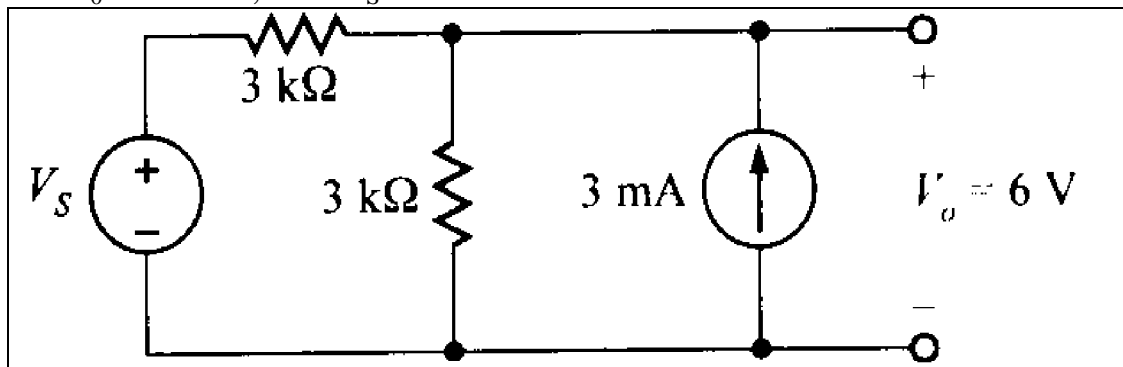2.55 Give $V_o = 6 \text{ Volts}$, find V_S .



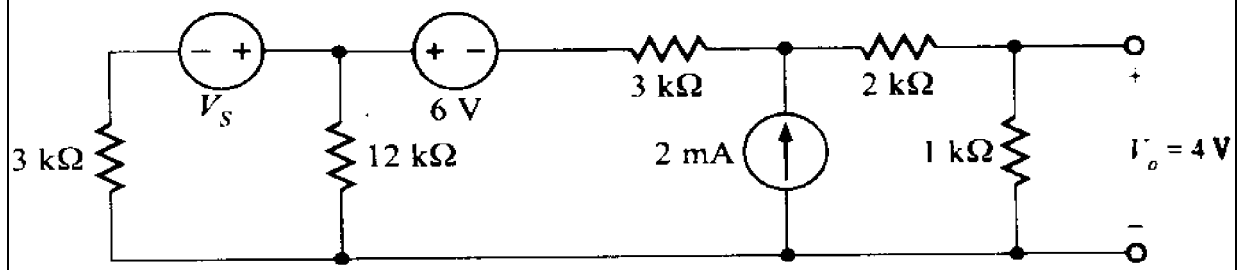2.58. Given that $V_o = 4 \text{ V}$ in the network in Fig. P2.58, find V_S .



2.65. Find V_o in the circuit in Fig. P2.65.

