

# EECS 215: Introduction to Electronic Circuits FA24

## Homework Set 5

Issued: 10/4/24

Due: 10/11/24, 5:00 PM submitted electronically on Gradescope.


### Contents

Problem 1. UMF P2.71 with additions .....	1
Problem 2. UMF P.3.93 with modifications. ....	2
Problem 3. UMF with additions/changes .....	3
Problem 4. MOSFET Differential Amplifier .....	3
Problem 5. UMF P3.83 .....	4
Problem 6. UMF P4.24 (with additions).....	5
Problem 7. UMF 4.36 .....	6
Problem 8. UMF 4.50 .....	7

### Problem 1. UMF P2.71 with additions.


- Use Matlab to generate the plots. Assume 0.7V for the voltage drop of a forward-biased diode.
- Simulate using LTSpice (see the diode example from HW03) and compare the results to part a.

**2.71** If the voltage source in the circuit of **Fig. P2.70(a)** generates the single triangular waveform shown in **Fig. P2.70(c)**, generate plots for  $i_1(t)$  and  $i_2(t)$ .

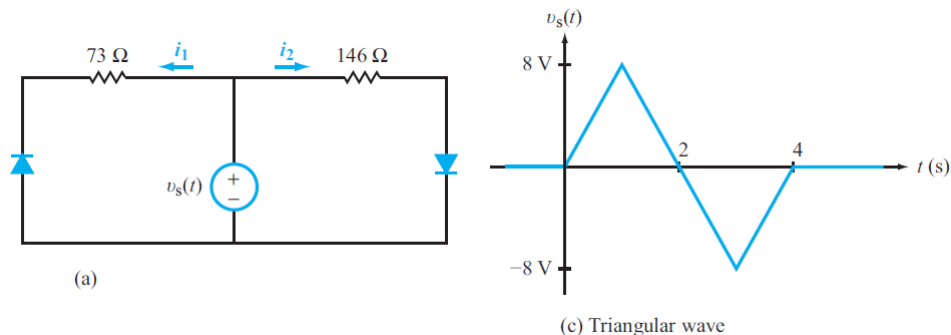

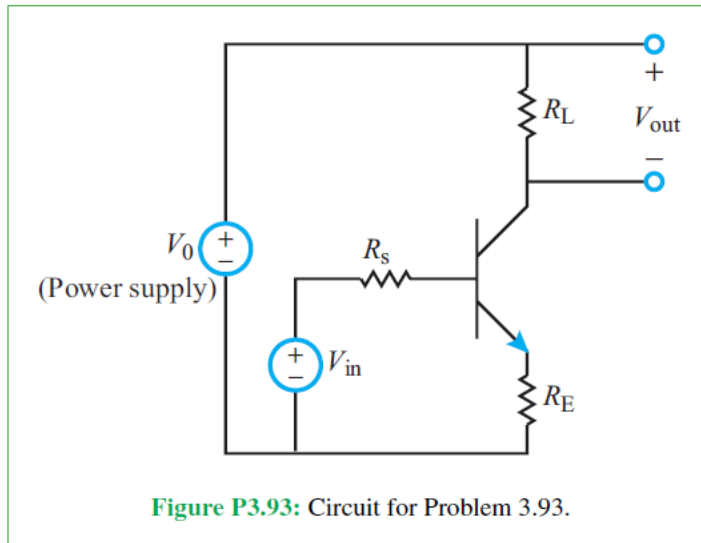Problem 2. UMF P.3.93 with modifications.


- Draw the linear circuit model for this circuit.
- Obtain an expression for  $V_{out}$  vs.  $V_{in}$  for the circuit below. Assume  $V_{BE} = 0.7V$  when the transistor is on and that we are interested in the regime  $V_{in} \geq 0.7V$
- What is the small signal gain of this circuit  $G = \frac{\partial V_{out}}{\partial V_{in}}$


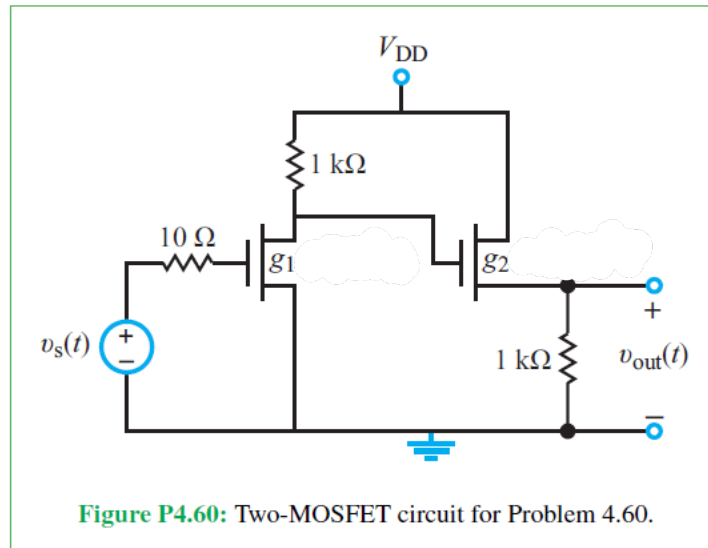
### Problem 3. UMF with additions/changes

- Do the problem as stated in the text but with the device transconductances changed to  $g_1 = g_2 = 20\Omega^{-1}$ . If needed, assume the MOSFET threshold voltage is 0.
- Find the Thevenin equivalent for this circuit as seen at the output.


**\*4.60** Determine  $v_{out}(t)$  as a function of  $v_s(t)$  for the circuit in Fig. P4.60. Assume  $V_{DD} = 2.5$  V.


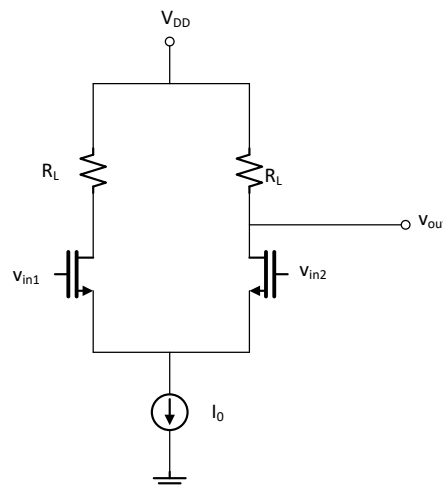
### Problem 4. MOSFET Differential Amplifier

Suppose we have the circuit shown below built with the idealized MOSFET covered in the text and class (UMF section 4-11). The two MOSFETs in the circuit are identical.


- Redraw the circuit using the linear equivalent circuit model for the idealized MOSFET.
- Using this picture, use nodal analysis to find a function relating  $v_{out}$  measure to ground vs.  $v_{in1}$ ,  $v_{in2}$  and the MOSFET transconductance ( $g$ ) and the other circuit constants.



### Problem 5. UMF P3.83

- Do the problem as stated in the text.
- Use LTSpice to simulate for  $V_{oc}$ ,  $I_{SC}$  and the circuit node voltages when the correct  $R_L$  is attached. Take the ground to be the negative terminal of the 15V voltage source.

**\*3.83** Determine the maximum power that can be extracted by the load resistor from the circuit in **Fig. P3.83**.

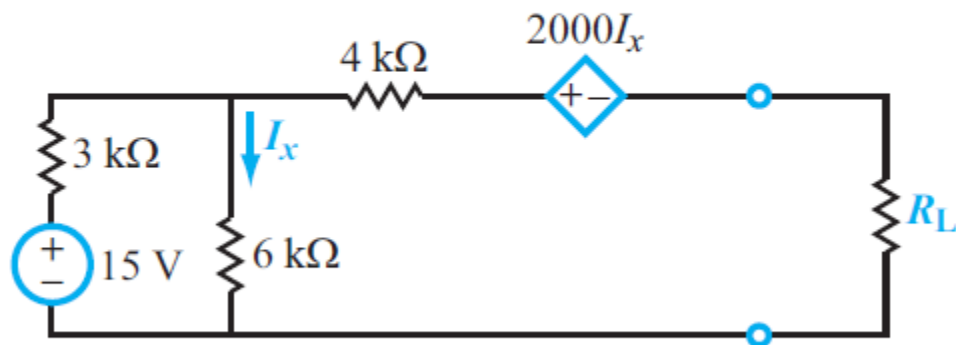


**Figure P3.83:** Circuit for Problem 3.83.

Problem 6. UMF P4.24 (with additions)

- Do the problem as stated.
- Find the limits on the linear range of  $v_s$  assuming we must have  $-15V \leq v_o \leq 15V$  due to the power supply limitations.


**4.24** For the circuit in Fig. P4.24, obtain an expression for voltage gain  $G = v_o/v_s$ .

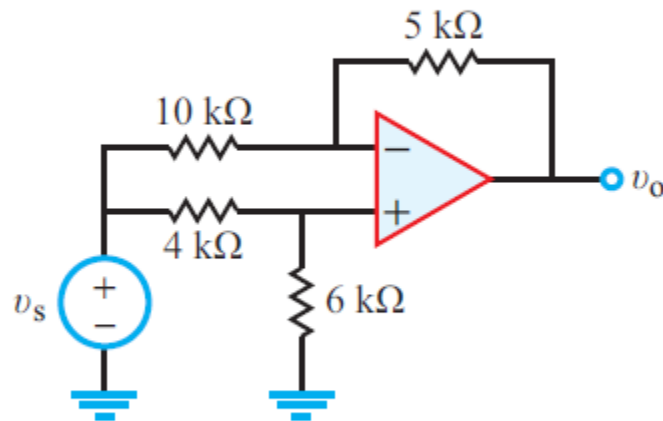

**Figure P4.24** Circuit for Problem 4.24.

Problem 7. UMF 4.36

**4.36** Find the value of  $v_o$  in the circuit in **Fig. P4.36**.

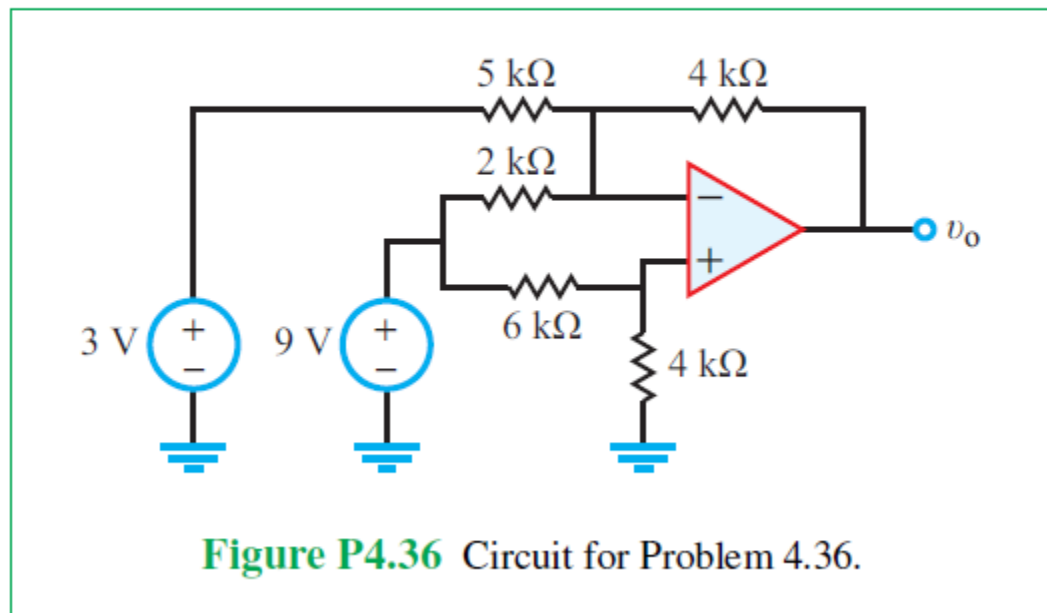

Problem 8. UMF 4.50

\* **4.50** Relate the output voltage  $v_o$  in **Fig. P4.50** to  $v_s$ .

